

Ohms Law I—Elementary DC Circuits with Light Bulbs

DATA SHEET

Part I.

4.

7.

8.

Part II.

3.

4.

5.

6.

7.

8.

9.

10.

11.

12.

Part III.

3.

4.

5.

6.

7.

8.

9.

10.

11.

12.

Part IV.

2. Your Prediction

3.

4.

5.

6.

7.

8.

9.

Part V.

2. Your Prediction

3.

4.

5.

6.

7.

8.

9.

Part VI.

2. Prediction:

3. Observation:

4. Explanation